


Digital logic and circuits Lab

[Section - C]

Group - 2

PROJECT TITLE

Implementation Of Fire Alarm System

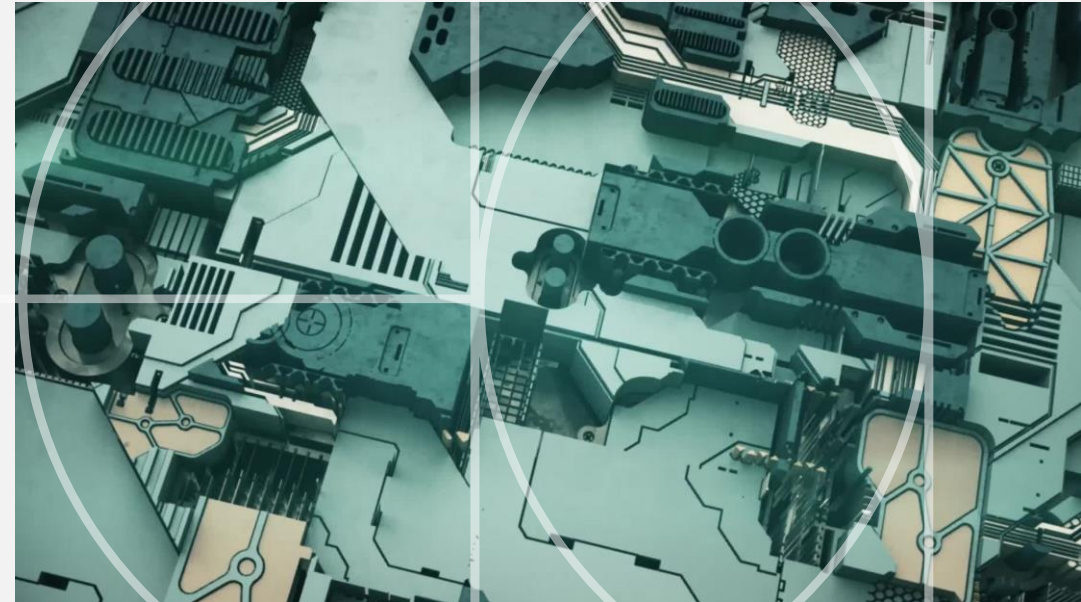

Group Members



NAME	ID	DEPARTMENT
Srabone Raxit	21-45038-2	CSE
Ahnaf Abdullah Zayad	21-45019-2	CSE
Safkat Khan	22-46392-1	CSE
Juhaer Al Mahbub	21-44687-1	CSE
Imtiaz Mahmud	20-43012-1	CSE

Table of contents

1. Abstract

2. Introduction

3. Equipment

4. Circuit
Diagram

5. Hardware
Implementation

6. Simulation

7. Working
Principle

8. Result

9. Discussion &
Conclusion

10. References

A large, solid orange circle serves as the background for the slide. The word "Abstract" is centered within this circle in a white, serif font. Below the word is a thin, white, slightly wavy horizontal line.

Abstract

Abstract

- The purpose of the project is to construct a circuit that can detect heat and trigger a periodic alarm when the heat reaches a certain temperature. The properties of 555 timer and thermistor was used to construct the circuit. The heat detection can alarm before the entire system catches fire or the rare and costly electronic components gets damaged beyond repair so that the damage due to overheat remains none to minimal.



Introduction



Introduction



While running, in a machine, many electrical and mechanical components get heated



Overheat can damage electrical or mechanical components beyond repair



Overheat can start fire



Heat detector circuit can alarm when the heat reaches a certain temperature



It can prevent damage and massive fire

Equipments






The Equipments-

Component Name	Quantity
Resistor 10K Ω	3
Resistor 15K Ω	1
Resistor 1K Ω	1
Resistor 100K Ω	1
IC NE555P	1
Capacitor 10 μ F	1
Capacitor 0.1 μ F	1
Thermistor 10K Ω	1
DC Power Supply (9V)	1
Connecting Wires	-
Breadboard	-

Circuit diagram

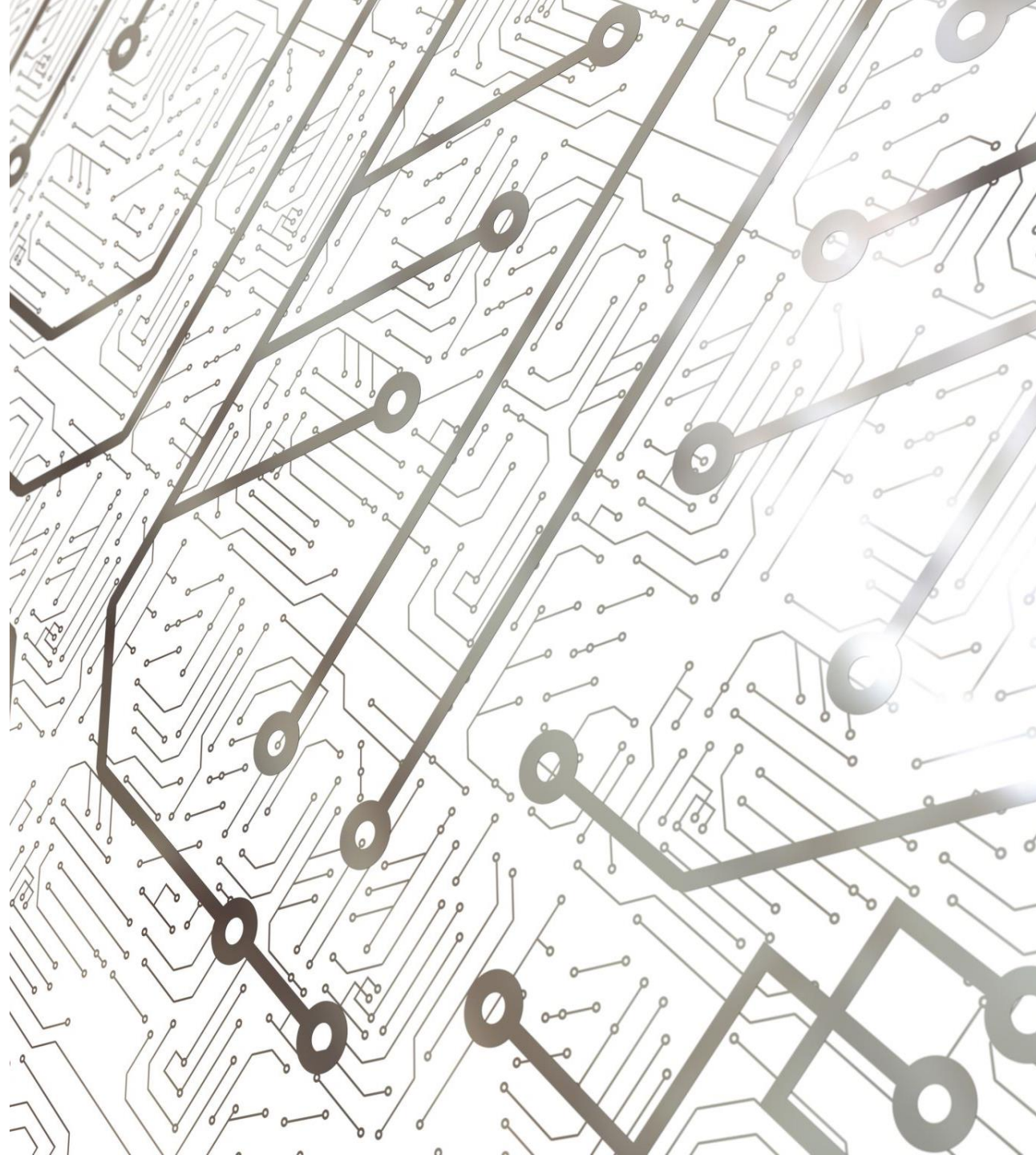

Circuit diagram

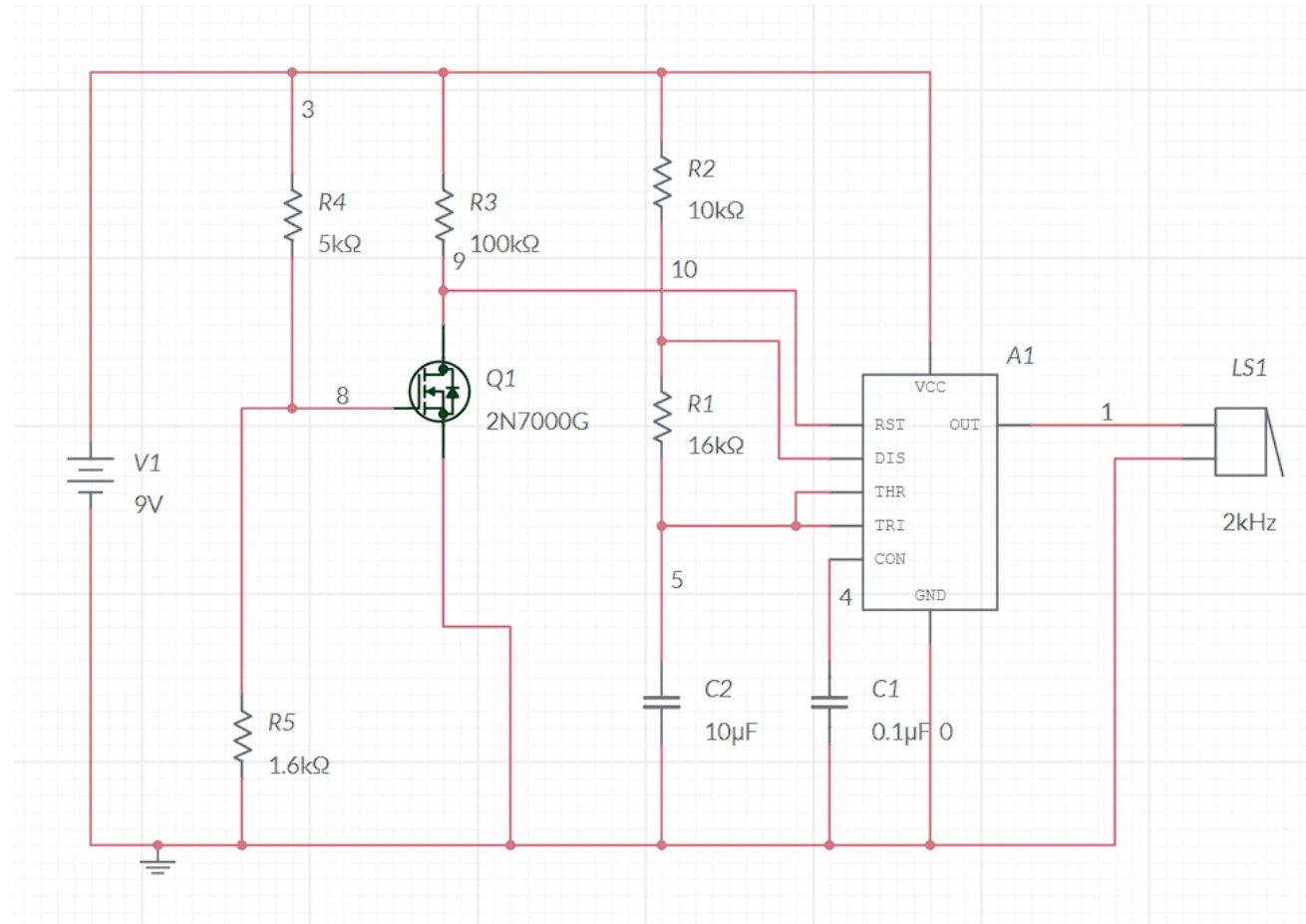





Figure: Heat and Fire Detection circuit using thermistor and 555 timer



Hardware Implementation



Hardware Implementation

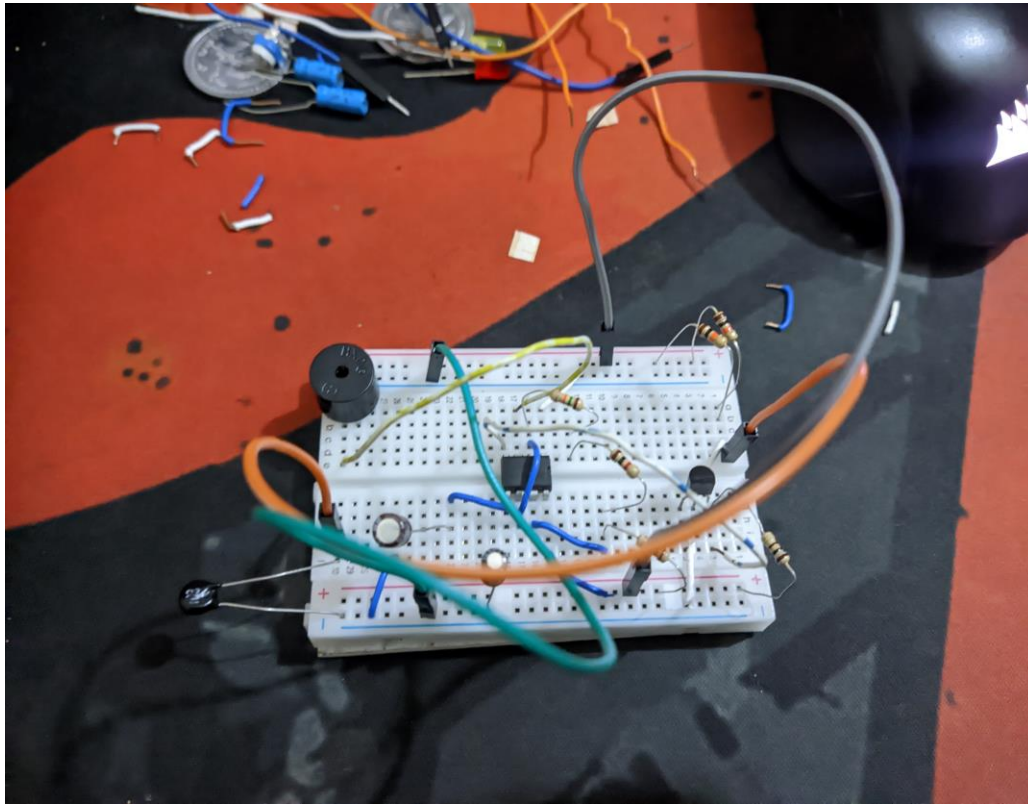


Fig: Top View


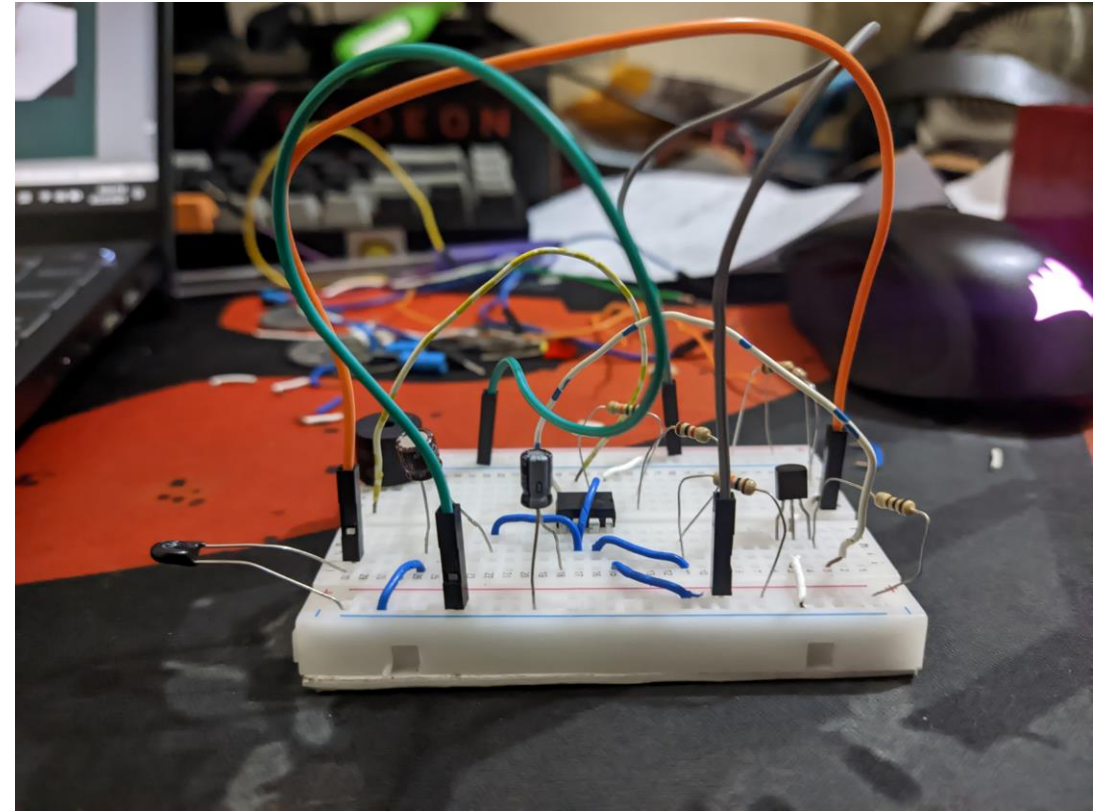


Fig: Front View

Hardware Implementation(Video)

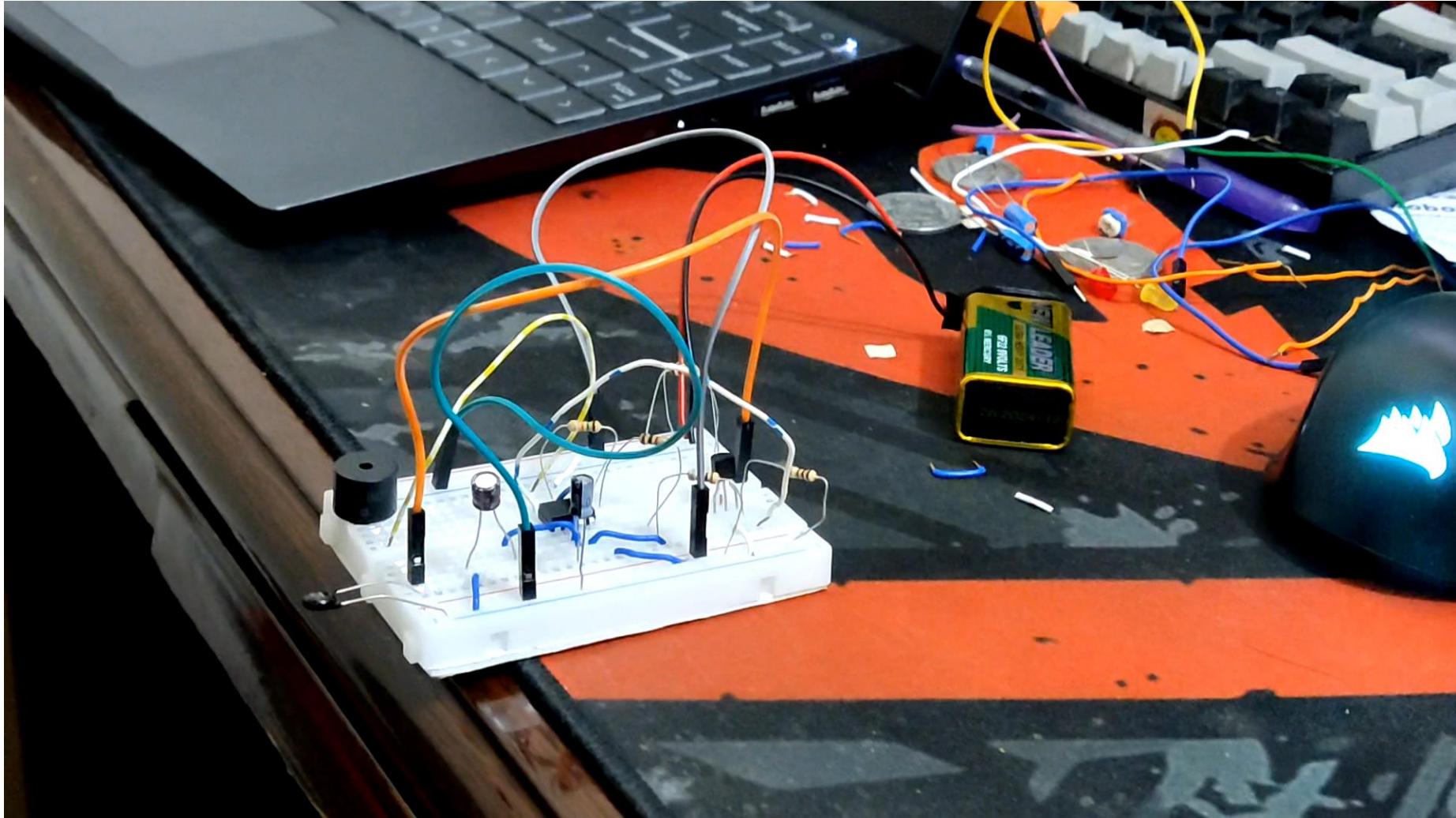



Simulation

Simulation

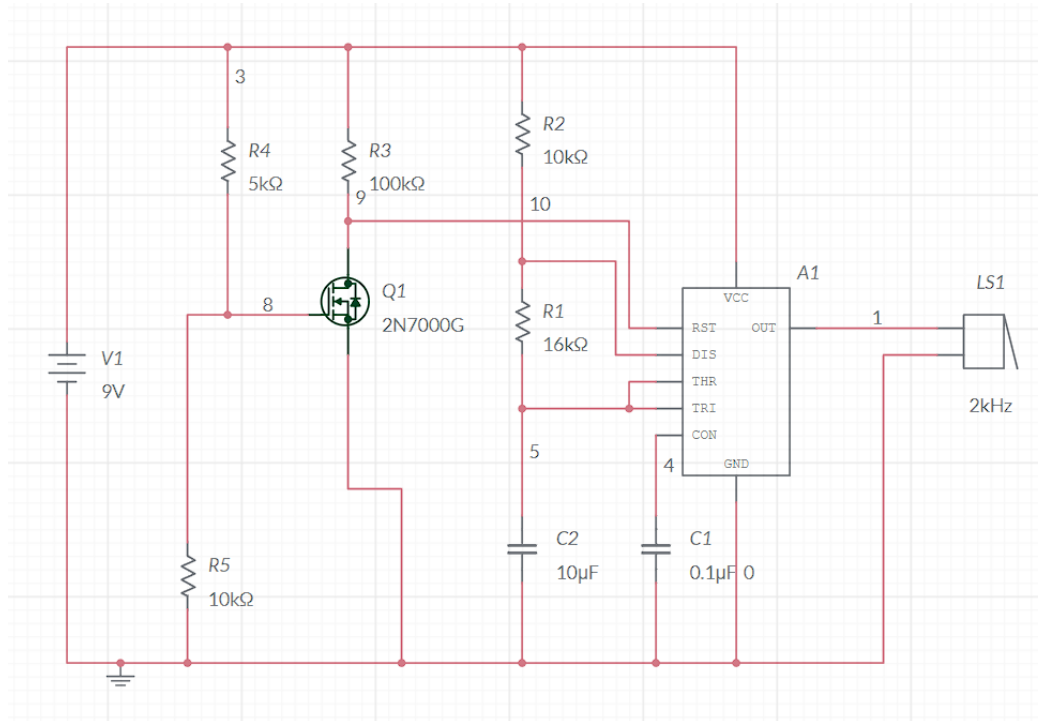


Fig: Thermistor at room temperature(25°C) and Buzzer inactive


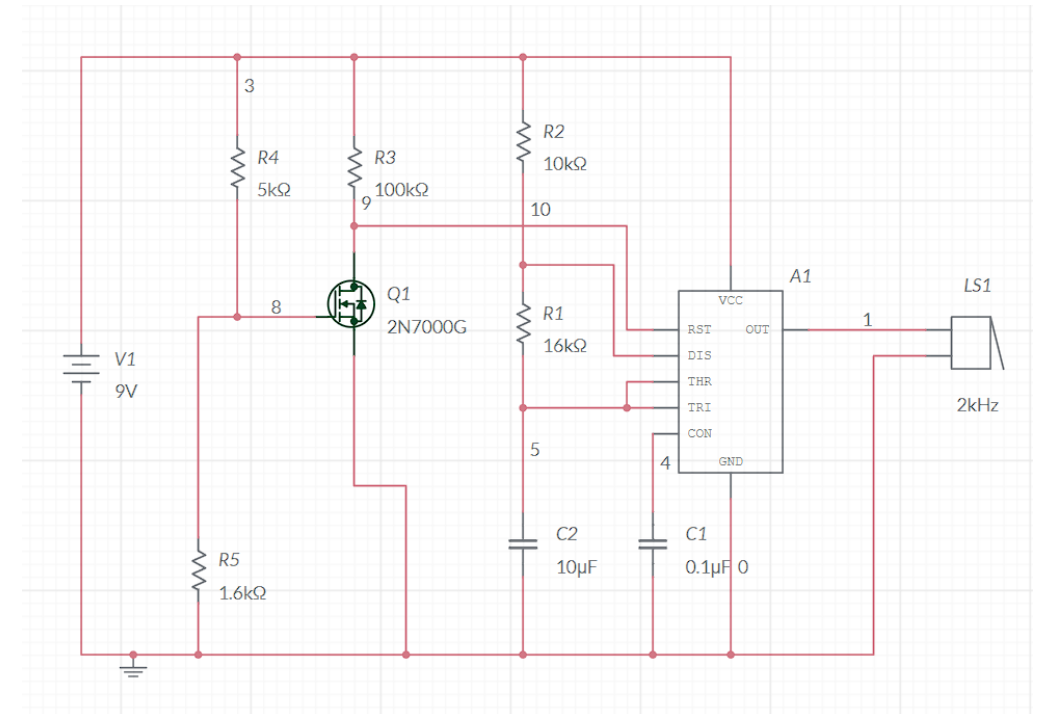


Fig: Thermistor Heated(70°C-75°C) and buzzer active

Working Principle

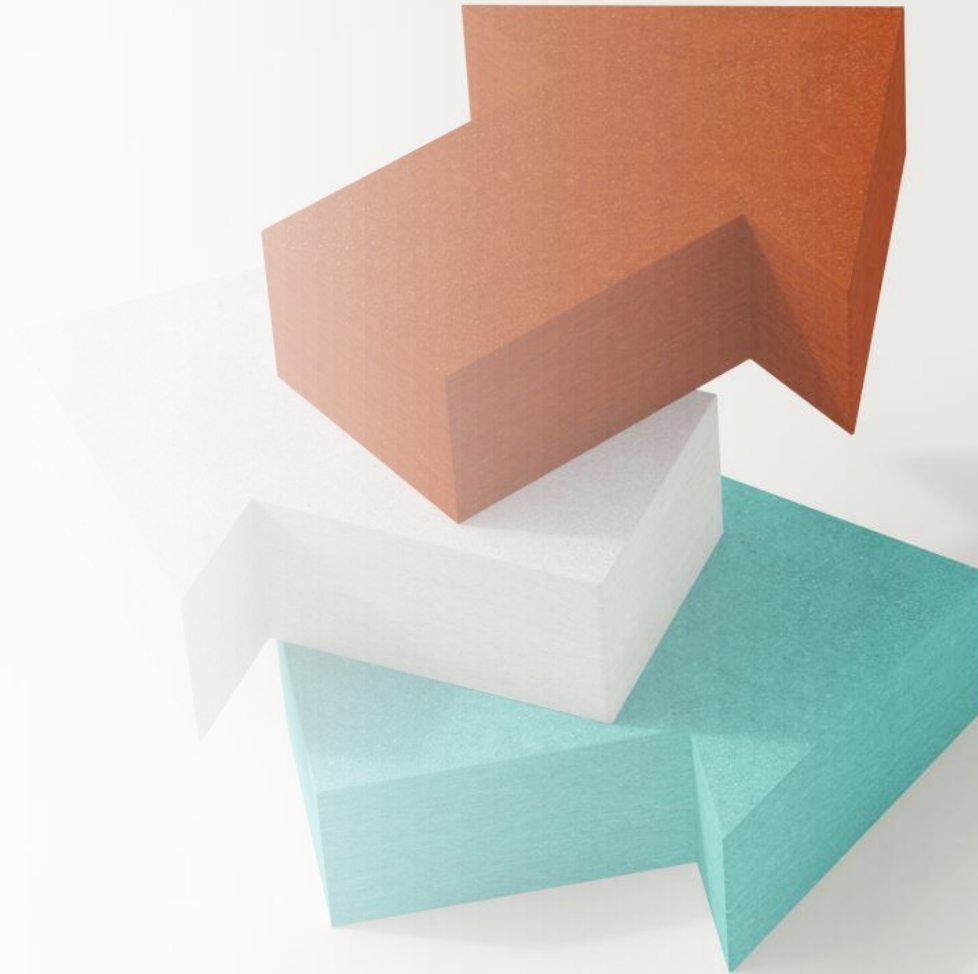

Working Principle

- Astable Multivibrator that would make the buzzer buzz periodically
- Reset receives input 0 the IC remains inactive

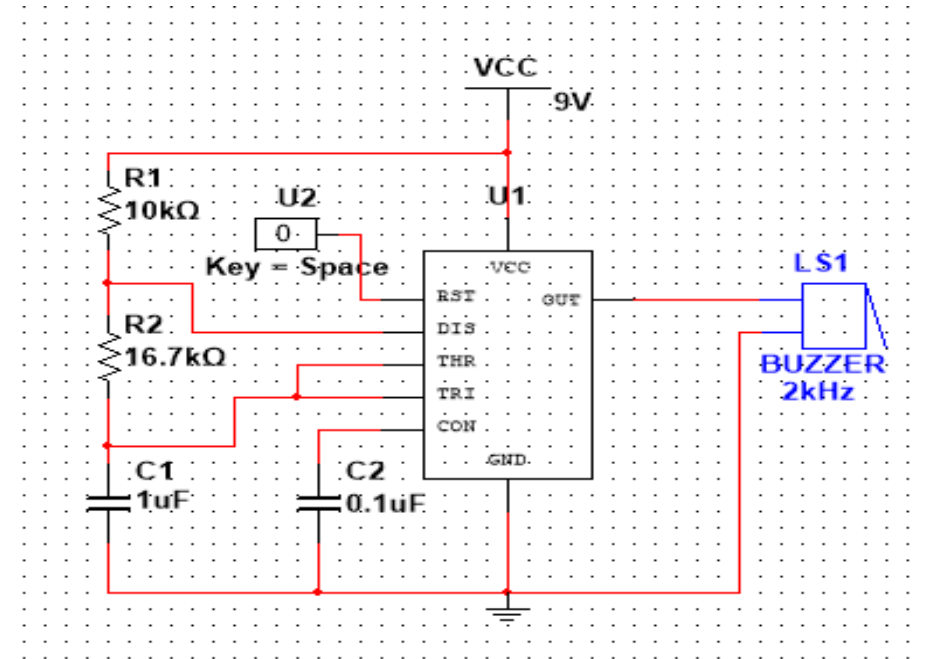


Fig: Astable Multivibrator

Working Principle(Cont.)

- Astable Multivibrator that would make the buzzer buzz periodically
- Reset receives input 1 the IC gets activated
- Property: IC active/inactive based on Reset input

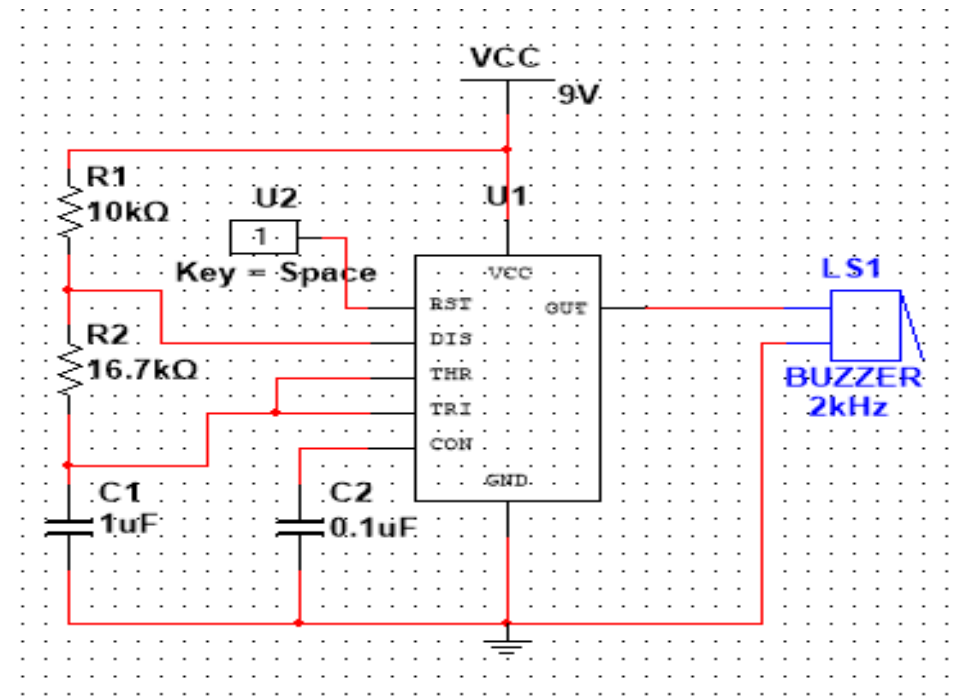


Fig: Astable Multivibrator

Working Principle(Cont.)

- Heat Detection Property
- Thermistor (NTC MF-52 100K Ω)
- Property: Temperature increase causes its resistance to decrease

T(°C)	R _t	B	R ₂₅
			10 K Ω
			3950
-30			181.70
-25			133.30
-20			98.88
-15			74.10
-10			56.06
-5			42.80
0			98.96
5			25.58
10			20.00
15			15.76
20			12.51
25			10.00
30			8.048
35			6.518
40			5.312
45			4.354
50			3.588
55			2.974
60			2.476
65			2.072
70			1.743
75			1.473
80			1.250
85			1.065
90			0.911
95			0.7824
100			0.6744
105			0.5836
110			0.5066

Specification Chart for NTC MF-52 100K Ω

Working Principle(Cont.)

- NMOS Inverter with Resistive Load

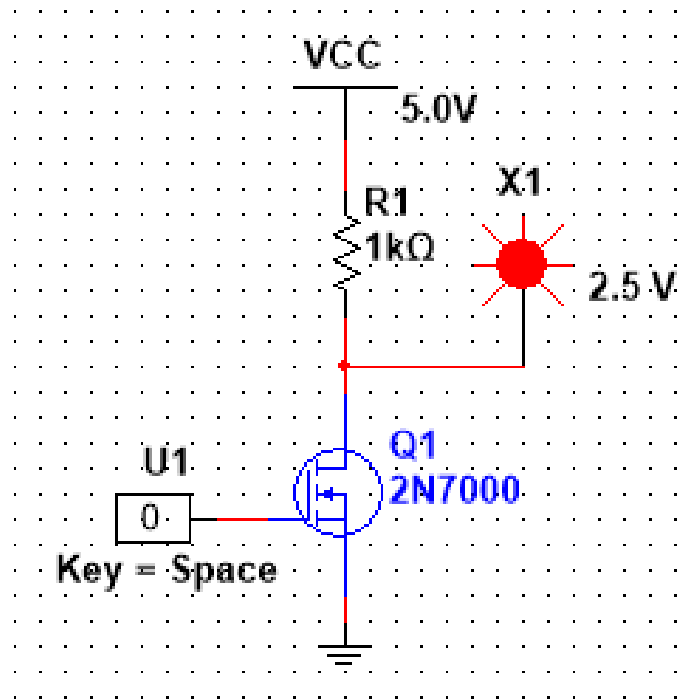


Fig: Inverter input = 1, Output = 0

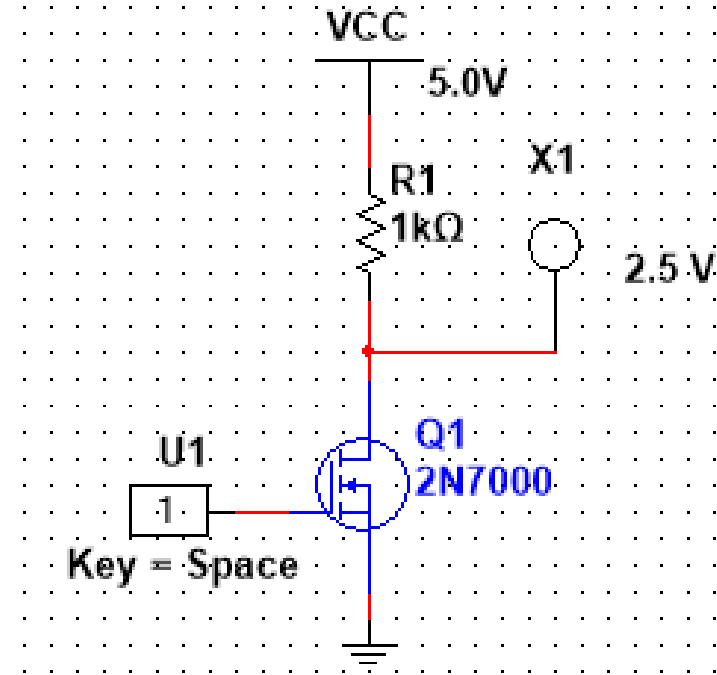


Fig: Inverter input = 0, Output = 1

Working Principle(Cont.)

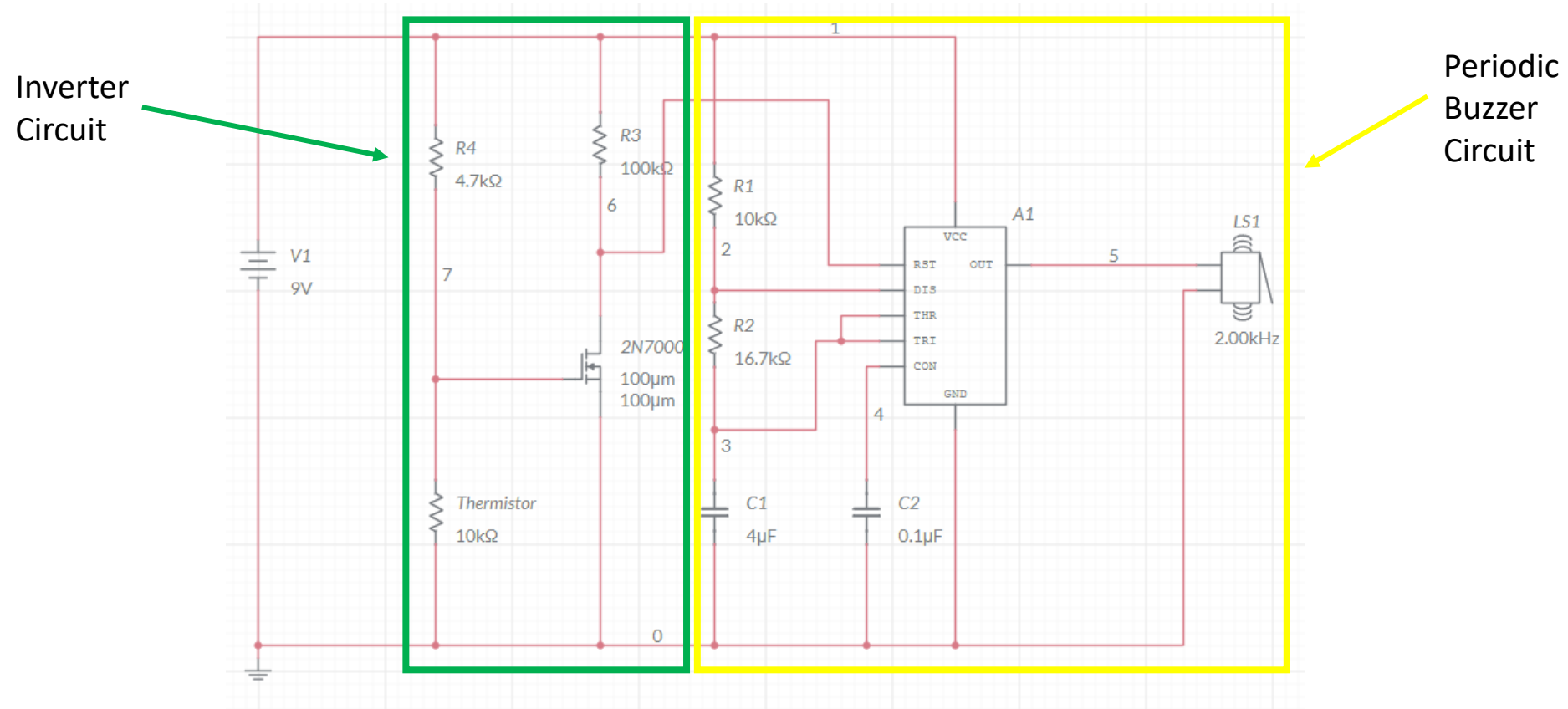


Fig: Final Circuit

WORKING PRINCIPLE

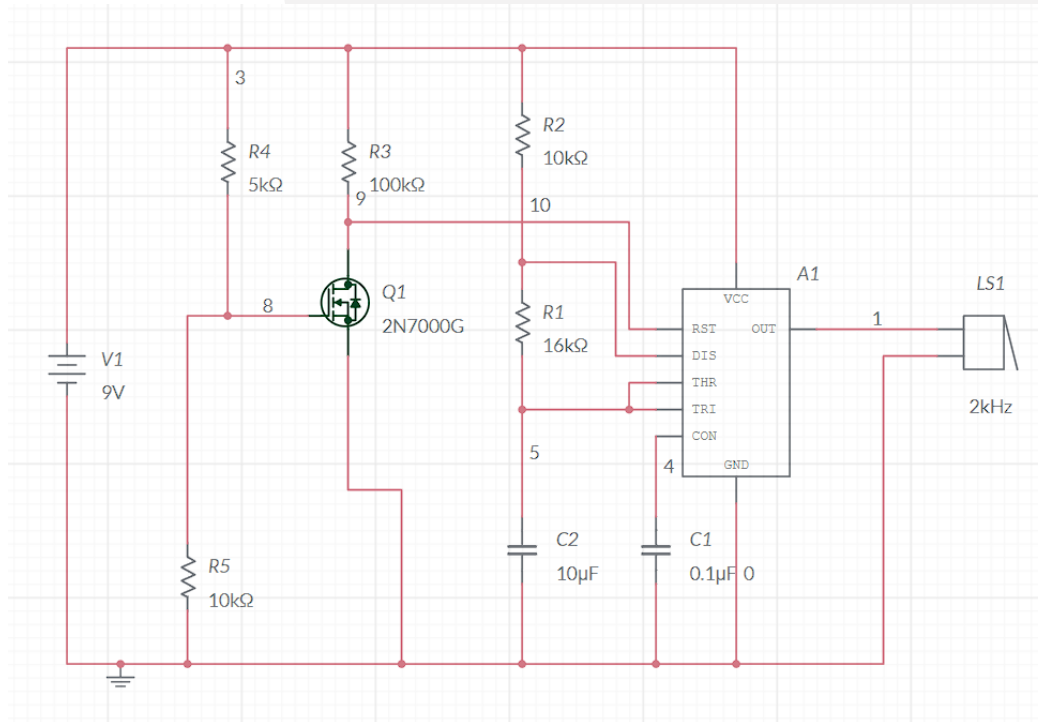


Fig: Thermistor at room temperature(25°C) and Buzzer inactive


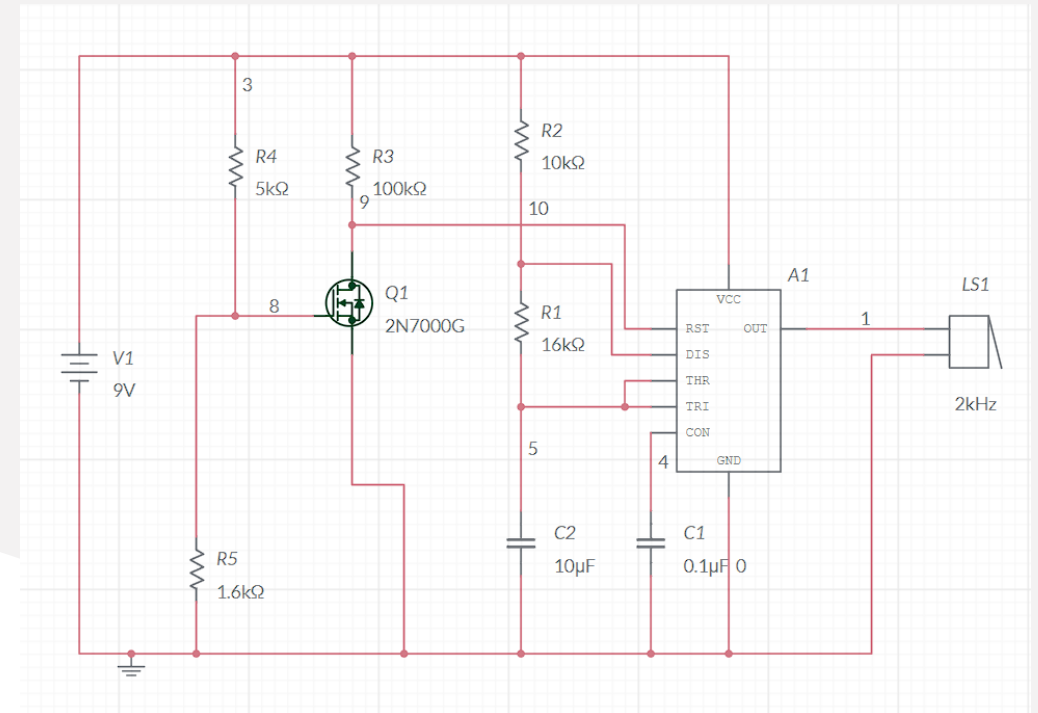



Fig: Thermistor Heated(70°C-75°C) and buzzer active

Result

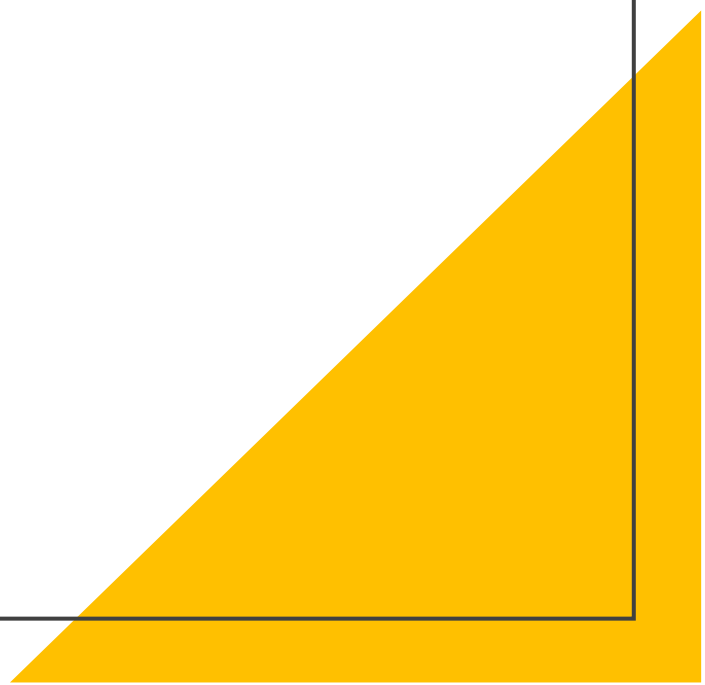



Result


- The designed circuit will alarm when the thermistor gets heated and its temperature reaches 70°C-75°C
- The buzzer will not get triggered if the temperature of the thermistor is below 70°C
- The buzzer receives periodic voltage from the 555 timer and buzzes periodically
- Result: The heat detection project circuit triggers periodic buzzer when the wanted temperature gets above 70°C



Discussion & Conclusion



Discussion & Conclusion

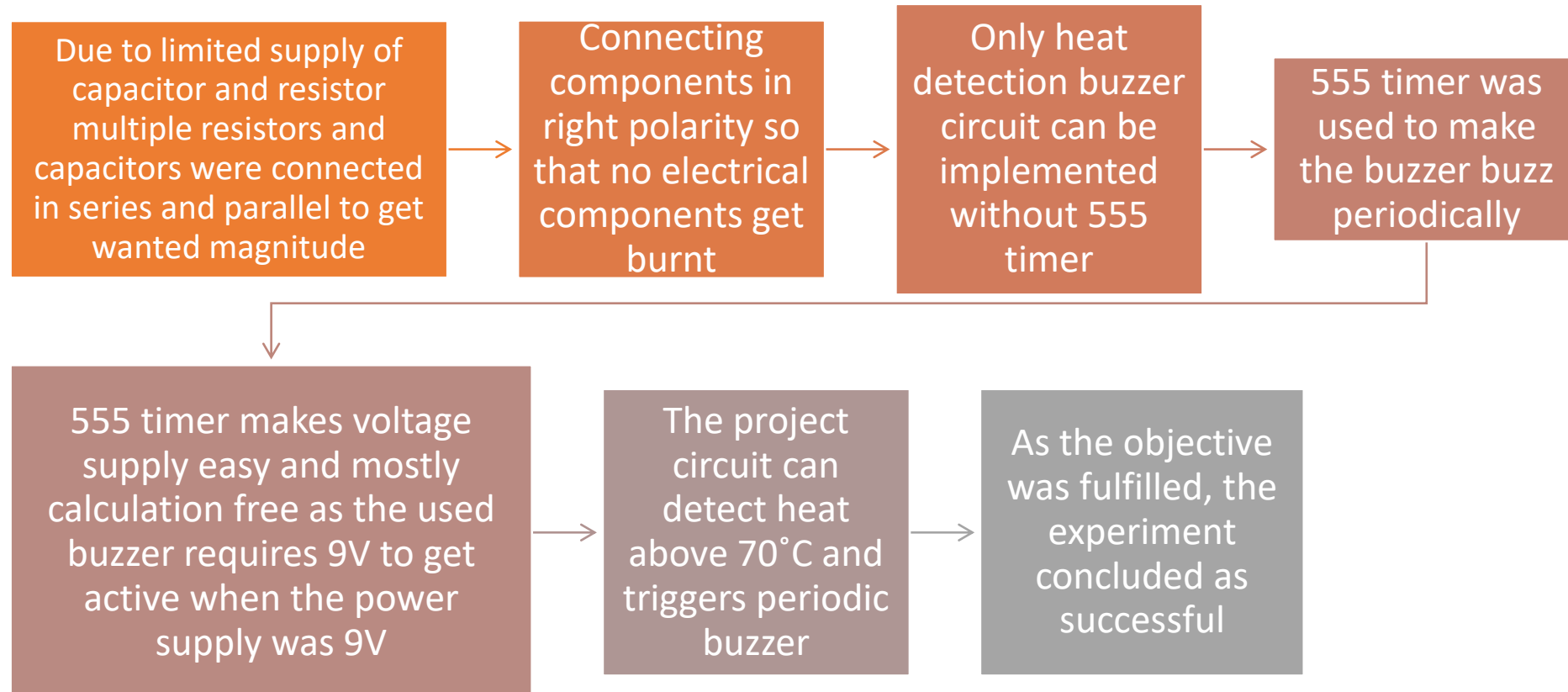



Thank You

Reference

1. Boylestad, Robert L., and Louis Nashelsky. Electronic Devices And Circuit Theory, 2006, Pearson Prentice Hall.

2. Thomas L. Floyd, Digital Fundamentals, 9th Edition, 2006, Prentice Hall.